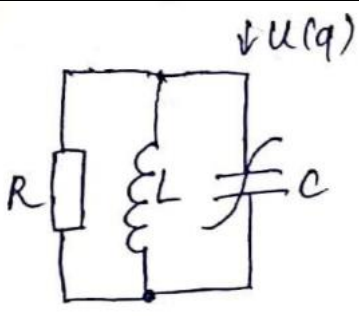
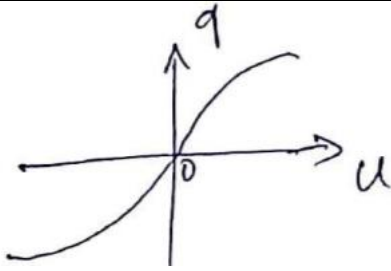
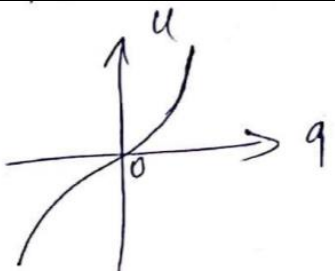
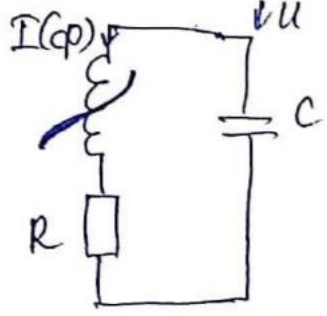
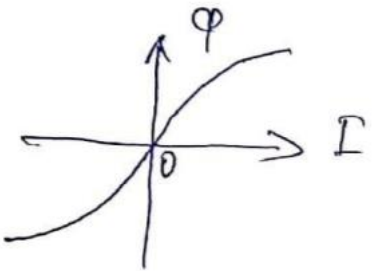
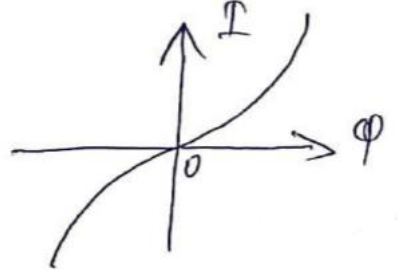


help for solving the problem...

case A

circuit	$q(U)$ dependence	$U(q)$ dependence
		
$I_C = \frac{dq}{dt} ;$ $I_R = \frac{U(q)}{R} ;$ $U_R = U_L = U_C = U(q)$ $U(q) = U_L = L \cdot \frac{dI_L}{dt} \rightarrow \frac{dI_L}{dt} = \frac{U(q)}{L}$ $I_R + I_L + I_C = 0$ $\frac{U(q)}{R} + I_L + \frac{dq}{dt} = 0$ <p>→ Further, it is easy to obtain a differential equation in the known form of a nonlinear oscillator</p>		

case B

circuit	$\Phi(I)$ dependence	$I(\Phi)$ dependence
		

$$I(\varphi) = I_C = C \cdot \frac{du_C}{dt} \rightarrow \frac{du_C}{dt} = \frac{I(\varphi)}{C}$$

$$u_L + u_R + u_C = 0 \rightarrow \frac{d\varphi}{dt} + I(\varphi) \cdot R + u_C = 0$$

→ Further, it is easy to obtain a differential equation in the known form of a nonlinear oscillator